

# Assignment 2


## Majority Gate

A majority gate will only output a 1 if more than 50% of the inputs are 1.

Majority Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Diagram

 

Design.sv

```
module majority_gate (input a, b, c, output y);  
    assign y = (a & b) | (a & c) | (b & c);  
endmodule
```

Testbench.sv


```
module test();  
    reg a, b, c;  
    wire y;  
  
    majority_gate TEST (.a(a), .b(b), .c(c), .y(y));  
endmodule
```

```

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
    a = 0; b = 0; c = 0; #10;
    a = 0; b = 1; c = 0; #10;
    a = 0; b = 0; c = 1; #10;
    a = 1; b = 1; c = 0; #10;
    a = 1; b = 0; c = 1; #10;
    a = 0; b = 1; c = 1; #10;
    a = 1; b = 1; c = 1; #10;
end
endmodule

```

Waveform

 


## Full Adder

A full adder adds two 1-bit inputs, plus a carry bit. It outputs the sum. The second output bit is a carry bit that can be chained to another full adder.

Full Adder Table

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Diagram

 

Design.sv

```
module full_adder(input a, b, c_in, output sum, c_out);
    wire h1_sum, h1_carry, h2_carry;
    half_adder had1 (.a(a), .b(b), .sum(h1_sum), .carry(h1_carry));
    half_adder had2 (.a(h1_sum), .b(c_in), .sum(sum), .carry(h2_carry));
    assign c_out = h1_carry | h2_carry;
endmodule


module half_adder (input a, b, output sum, carry);
    assign sum = a ^ b;
    assign carry = a & b;
endmodule
```

Testbench.sv

```
module test();
    reg a, b, c_in;
    wire sum, c_out;
    full_adder TEST (.a(a), .b(b), .c_in(c_in), .sum(sum), .c_out(c_out));

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
        a = 0; b = 0; c_in = 0; #10;
        a = 0; b = 1; c_in = 0; #10;
        a = 0; b = 0; c_in = 1; #10;
        a = 1; b = 1; c_in = 0; #10;
        a = 1; b = 0; c_in = 1; #10;
        a = 0; b = 1; c_in = 1; #10;
        a = 1; b = 1; c_in = 1; #10;
    end
endmodule
```

## Waveform

 


## 4:16 Encoder

Takes in a 4bit input and outputs 16bits. The 16bit output has 1 high and the rest low. The position of the 1 is dependent on the 4bit number. 0000 gives 0000000000000001, 0001 shifts left by one position 0000000000000010 and 1111 gives 1000000000000000.

4:16 Encoder Table

ABCD	Y0-Y15
0000	0000000000000001
0001	0000000000000010
0010	0000000000000100
0011	0000000000001000
0100	0000000000010000
0101	0000000000100000
0110	0000000001000000
0111	0000000010000000
1000	0000000100000000
1001	0000001000000000
1010	0000010000000000
1011	0000100000000000
1100	0001000000000000
1101	0010000000000000
1110	0100000000000000
1111	1000000000000000

## Diagram

 

Design.sv

```
module encoder416(input [3:0] in, output reg [15:0] out);
  always @ (in) begin
    case (in)
      4'b0000: out = 16'b0000000000000001;
      4'b0001: out = 16'b0000000000000010;
      4'b0010: out = 16'b0000000000000100;
      4'b0011: out = 16'b0000000000001000;
      4'b0100: out = 16'b0000000000010000;
      4'b0101: out = 16'b0000000000100000;
      4'b0110: out = 16'b0000000001000000;
      4'b0111: out = 16'b0000000010000000;
      4'b1000: out = 16'b0000000100000000;
      4'b1001: out = 16'b0000001000000000;
      4'b1010: out = 16'b0000010000000000;
      4'b1011: out = 16'b0000100000000000;
      4'b1100: out = 16'b0001000000000000;
      4'b1101: out = 16'b0010000000000000;
      4'b1110: out = 16'b0100000000000000;
      4'b1111: out = 16'b1000000000000000;
      default: out = 16'b0000000000000001;
    endcase
  end
endmodule
```

Testbench.sv


```
module test();
  reg [3:0] in;
  wire [15:0] out;
  encoder416 TEST (.in(in), .out(out));
endmodule
```

```

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
    in = 4'b0000; #5;
    in = 4'b0001; #5;
    in = 4'b0010; #5;
    in = 4'b0011; #5;
    in = 4'b0100; #5;
    in = 4'b0101; #5;
    in = 4'b0110; #5;
    in = 4'b0111; #5;
    in = 4'b1000; #5;
    in = 4'b1001; #5;
    in = 4'b1010; #5;
    in = 4'b1011; #5;
    in = 4'b1100; #5;
    in = 4'b1101; #5;
    in = 4'b1110; #5;
    in = 4'b1111; #5;
end
endmodule

```

Waveform

 

## Multiplexer and Demultiplexer


A multiplexer takes inputs A, B, C, D, S0 and S1. It's a data selector. The 2bit value of S0 and S1 from 00 to 11 determines which of A, B, C and D is the output.

A demultiplexer takes inputs Data, S0 and S1. The 2bit value of S0 and S1 from 00 to 11 determines which if the outputs Y0, Y1, Y2 and Y3 is high.

Multiplexer and Demultiplexer Table

Inputs					Outputs				
A	B	C	D	Data	Out	Y0	Y1	Y2	Y3
Choice	S0		S1		Out	Y0	Y1	Y2	Y3
1	0		0		A	X	X	X	X
1	0		1		B	X	X	X	X
1	1		0		C	X	X	X	X
1	1		1		D	X	X	X	X
0	0		0		X	Data	0	0	0
0	0		1		X	0	Data	0	0
0	1		0		X	0	0	Data	0
0	1		1		X	0	0	0	Data

Diagram

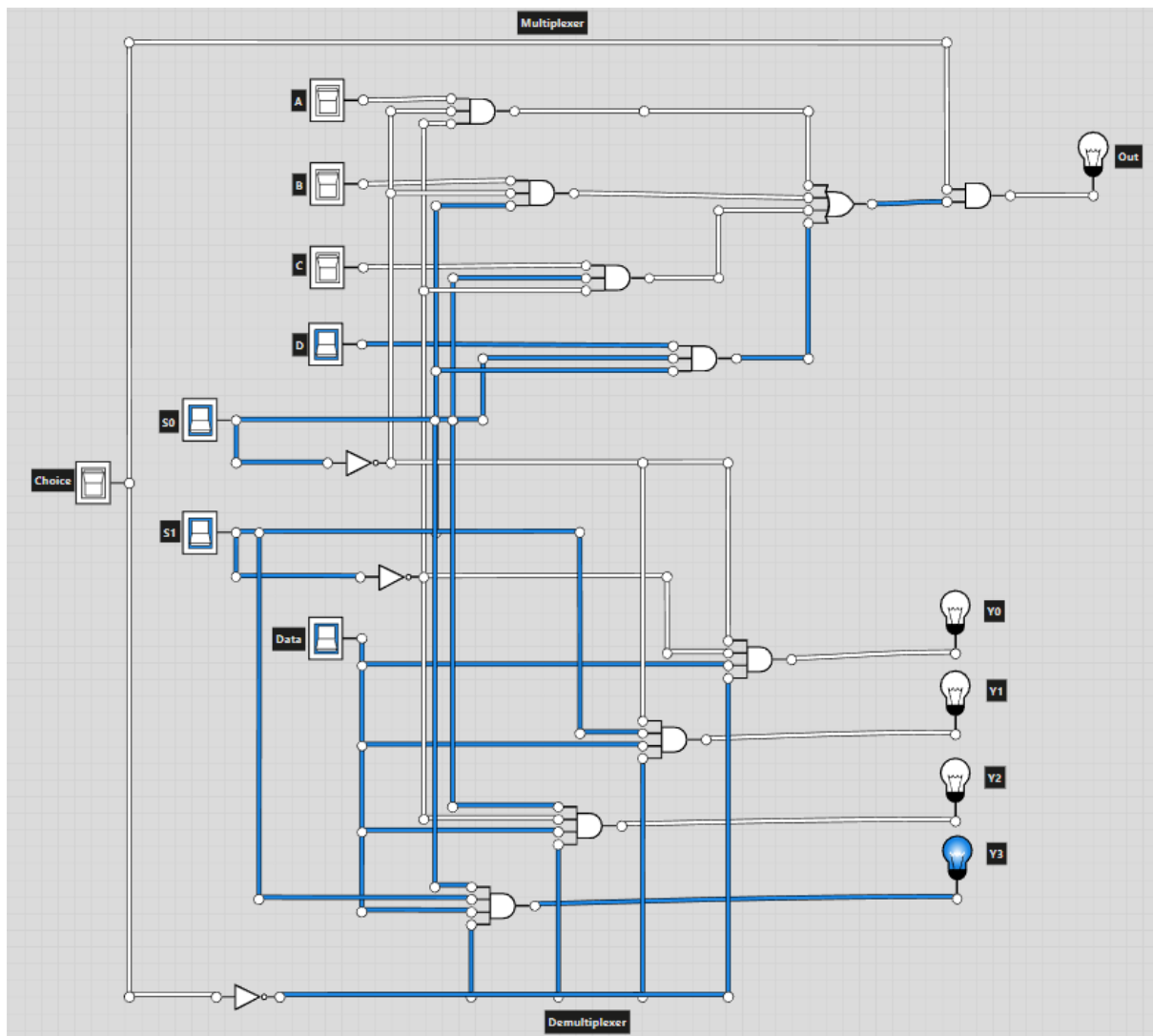

Design.sv

```
module mux_demux (input choice, a, b, c, d, data, s0, s1,
                  output out, y0, y1, y2, y3);
    reg out, y0, y1, y2, y3;
    always @(*) begin
        if (choice == 1) begin // multiplexer
            case ({s0,s1})
                {1'b0,1'b0}: out = a;
                {1'b0,1'b1}: out = b;
                {1'b1,1'b0}: out = c;
                {1'b1,1'b1}: out = d;
            endcase
        end
        else begin // demultiplexer
            case ({s0,s1})
                {1'b0,1'b0}: y0 = data;
            endcase
        end
    end
end
```

```

        {1'b0,1'b1}: y1 = data;
        {1'b1,1'b0}: y2 = data;
        {1'b1,1'b1}: y3 = data;
    endcase
end
end
endmodule

```

## Testbench.sv

```

module test();
    reg choice, a, b, c, d, data, s0, s1;
    wire out, y0, y1, y2, y3;

    mux_demux TEST (.choice(choice), .a(a), .b(b), .c(c), .d(d), .data(data),
                    .s0(s0), .s1(s1),
                    .out(out), .y0(y0), .y1(y1), .y2(y2), .y3(y3));


    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
        choice = 1; a = 0; s0 = 1'b0; s1 = 1'b0; #5;
        choice = 1; a = 1; s0 = 1'b0; s1 = 1'b0; #5;
        choice = 1; b = 0; s0 = 1'b0; s1 = 1'b1; #5;
        choice = 1; b = 1; s0 = 1'b0; s1 = 1'b1; #5;
        choice = 1; c = 0; s0 = 1'b1; s1 = 1'b0; #5;
        choice = 1; c = 1; s0 = 1'b1; s1 = 1'b0; #5;
        choice = 1; d = 0; s0 = 1'b1; s1 = 1'b1; #5;
        choice = 1; d = 1; s0 = 1'b1; s1 = 1'b1; #5;
        choice = 0; data = 0; s0 = 1'b0; s1 = 1'b0; #5;
        choice = 0; data = 1; s0 = 1'b0; s1 = 1'b0; #5;
        choice = 0; data = 0; s0 = 1'b0; s1 = 1'b1; #5;
        choice = 0; data = 1; s0 = 1'b0; s1 = 1'b1; #5;
        choice = 0; data = 0; s0 = 1'b1; s1 = 1'b0; #5;
        choice = 0; data = 1; s0 = 1'b1; s1 = 1'b0; #5;
        choice = 0; data = 0; s0 = 1'b1; s1 = 1'b1; #5;
        choice = 0; data = 1; s0 = 1'b1; s1 = 1'b1; #5;

    end
endmodule

```



## Waveform

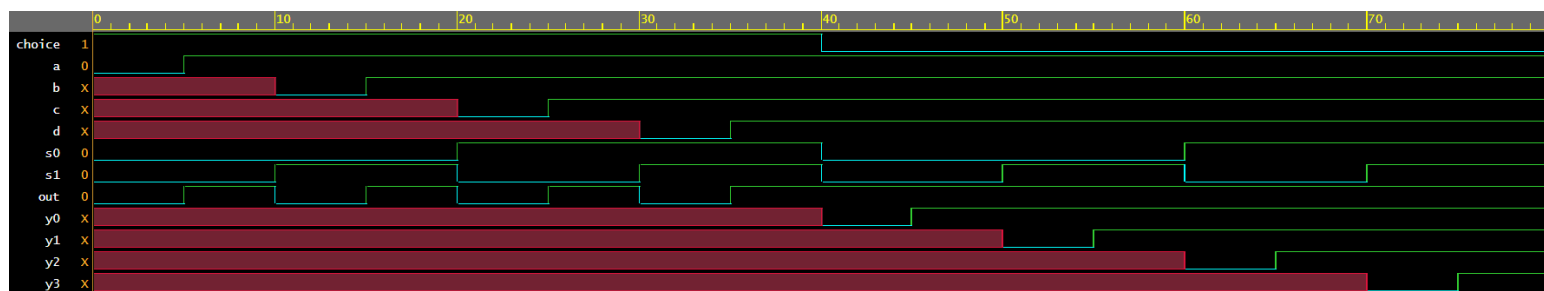

## Downcounter

Downcounter counts to 0 from any value. When reset is high, the counter starts from its max value and each clock cycle, the counter value is decremented by 1 and the output is updated to reflect the new count value.

### Design.sv

```
module down_counter(input clk, reset, output[15:0] counter);
    reg [15:0] counter_down;

    always @(posedge clk or posedge reset)
    begin
        if(reset)
            counter_down <= 16'b1111111111111111;
        else
            counter_down <= counter_down - 16'b0000000000000001;
        end

    assign counter = counter_down;
endmodule
```

### Testbench.sv

```
module test();
    reg clk, reset;
    wire [15:0] counter;
    down_counter Test(clk, reset, counter);
    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
        clk=0;
        //forever #5 clk=~clk;
        #5 clk=~clk;
        #5 clk=~clk;
        #5 clk=~clk;
        #5 clk=~clk;
    end
endmodule
```

```

#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
#5 clk=~clk;
end
initial begin
    reset=1;
    #10;
    reset=0;
end
endmodule

```

Waveform

