

Assignment 1


XOR Gate

XOR gate will only output a 1 if the 2 inputs are different. For example if A is a 1 and B is 0, then C will be a 1. If A and B are the same, then C will be 0.

XOR Table

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

XOR diagram

 

design.sv

```
module xor_gate(input a,b, output c);  
    assign c = a^b;  
  
endmodule
```

testbench.sv

```
module test;  
    reg a,b;  
    wire c;
```


```

xor_gate TEST(.a(a), .b(b), .c(c));

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
    a=0;
    b=0;
    #10
    a=1;
    b=0;
    #10
    a=0;
    b=1;
    #10
    a=1;
    b=1;
    #10;
end
endmodule

```

waveform

 


NAND Gate

NAND is the inverse of the AND gate. The AND gate output is 1 if all inputs are 1. NAND is the opposite, it's output is 1 unless all inputs are 1.

NAND Table

A	B	C	C'
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

NAND Diagram

 


design.sv

```
module nand_gate(input a,b, output c);  
    assign c = ~(a&b);  
  
endmodule
```

testbench.sv

```
module test;  
    reg a,b;  
    wire c;  
  
    nand_gate TEST(.a(a), .b(b), .c(c));  
  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1);  
        a=0;  
        b=0;  
        #10  
        a=1;  
        b=0;  
        #10  
        a=0;  
        b=1;  
        #10  
        a=1;  
        b=1;  
        #10;  
    end  
endmodule
```

waveform

 


NOR

NOR gate is the opposite of the OR gate. For OR, the output is 1 when any of its inputs are 1. For NOR, the output is 0 if any of its inputs are 1.

NOR Table

A	B	C	C'
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

NOR diagram

 

design.sv

```
module nor_gate(input a,b, output c);  
    assign c = ~(a|b);  
  
endmodule
```

testbench.sv

```
module test;  
    reg a,b;  
    wire c;
```


```

nor_gate TEST(.a(a), .b(b), .c(c));

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
    a=0;
    b=0;
    #10
    a=1;
    b=0;
    #10
    a=0;
    b=1;
    #10
    a=1;
    b=1;
    #10;
end
endmodule

```

Waveform

 


SR Flip Flop

SR flip flop is a synchronous circuit that has inputs S, R and clk. When S is 1, then Q is 1. When R is 1 then Qbar is 1.

Table

S	R	Q	Qbar
0	0	0	1
0	1	0	1
1	0	1	0
1	1	X	X

Diagram

 

design.sv

```
module srff(input s,r,clk, output q,qb);
  reg q,qb;

  initial
  begin
    q = 1'b1;
    qb = 1'b0;
  end

  always @(posedge clk or negedge clk)
  begin
    case ({s,r})
      {1'b0,1'b0}:
        begin
          q=q;
          qb=qb;
        end
      {1'b0,1'b1}:
        begin
          q=0;
          qb=1;
        end
      {1'b1,1'b0}:
        begin
          q=1;
          qb=0;
        end
      {1'b1,1'b1}:
    end
  end
```

```
        begin
            q=1'bx;
            qb=1'bx;
        end
    endcase
end
endmodule
```

testbench.sv


```
module Test;
    reg s;
    reg r;
    reg clk;

    wire q;
    wire qb;
    srff Test(.s(s), .r(r), .clk(clk), .q(q), .qb(qb));

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
        clk=0;
    end

    always #5 clk = ~clk;
    initial
        begin
            s=1;
            r=0;
            #10
            s=0;
            r=1;
            #10
            s=0;
            r=0;
            #10;
            s=1;
            r=1;
            #10;
            $finish;
        end
endmodule
```

Waveform

 


JK Flip Flop

If J and K are different, then when the clock is 1, it takes the value of J. If J and K are both 1 and the clock is 1, then the value of K is taken. Otherwise no change happens.

Table

J	K	Q	Qbar
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	1
0	1	1	0
1	0	1	1
1	1	1	0

Diagram

 

design.sv

```
module jkff(input j,k,clk, output q,qb);
    reg q,qb;

    initial
        begin
            q = 1'b1;
            qb = 1'b0;
        end

    always @(posedge clk or negedge clk)
        begin
            case ({j,k})
                {1'b0,1'b0}:
                    begin
                        q=q;
                        qb=qb;
                    end
                {1'b0,1'b1}:
                    begin
                        q=0;
                        qb=1;
                    end
                {1'b1,1'b0}:
                    begin
                        q=1;
                        qb=0;
                    end
                {1'b1,1'b1}:
                    begin
                        q=q;
                        qb=qb;
                    end
            endcase
        end
endmodule
```

testbench.sv

```
module Test;
    reg j;
    reg k;
    reg clk;

    wire q;
    wire qb;
```

```


jkff Test(.j(j), .k(k), .clk(clk), .q(q), .qb(qb));

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
    clk=0;
end

always #5 clk = ~clk;
initial
    begin
        j=1;
        k=0;
        #10
        j=0;
        k=1;
        #10
        j=0;
        k=0;
        #10;
        j=1;
        k=1;
        #10;
        $finish;
    end
endmodule

```

waveform

 

T Flip Flop


The state only changes when T is 1. When the clock is 0, q is 1 and qbar is 0, when the clock is 1, q is 0 and qbar is 1.

Table

T	Q	Qbar
0	0	0
1	0	1

0	1	1
1	1	0

Diagram

 

design.sv

```
module tff(input t,clk, output q,qb);
  reg q,qb;

  initial
  begin
    q = 1'b0;
    qb = 1'b1;
  end

  always @(posedge clk or negedge clk)
  begin
    case (t)
      {1'b0}:
        begin
```

```

        q=q;
        qb=qb;
    end
    {1'b1}:
    begin
        q=~q;
        qb=~qb;
    end
endcase
end
endmodule

```

testbench.sv

```

module Test;
    reg t;
    reg clk;

    wire q;
    wire qb;
    tff Test(.t(t), .clk(clk), .q(q), .qb(qb));

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
        clk=0;
    end

    always #5 clk = ~clk;
    initial
        begin
            t=0;
            #10
            t=1;
            #10
            t=0;
            #10;
            t=1;
            #10;
            $finish;
        end
endmodule

```

waveform

